

ECGR 5133

Final Project – Array Multiplier

Dr. Mukherjee

James Morar


Overview

The goal of this project was to lay out a pipelined, 8-bit array multiplier with a zero-skew clock network in a 0.6um process using Magic VLSI. The schematic below tersely summarizes how the multiplier is built. Each red square represents a DFF for pipelining. Y-values are the multiplicand, X-values are the multiplier, and Z-values are the outputs of the circuit. This project was done in three parts:


Part I – Unpipelined layout

Part II – Layout with DFF and without clock routing

 
Part III – Fully pipelined layout with zero-skew clock tree



For part III of the project, the zero-skew clock network was prototyped with the drawing below and then executed in layout. Each dot represents a flip-flop. Blue dots are the flip-flops which latch the z-values(outputs), orange dots latch y-values(multiplicand), red dots latch partial sums from the adders, and green dots latch the x-values(multiplier).

 


Part I – Non-Pipelined Layout

 

logic analyzer display			Zoom	Base	Window	Print
0.00						800.00
MULTPLICAND	87					
MULTIPLIER	229		115			
RESULT	 19923		 10005			

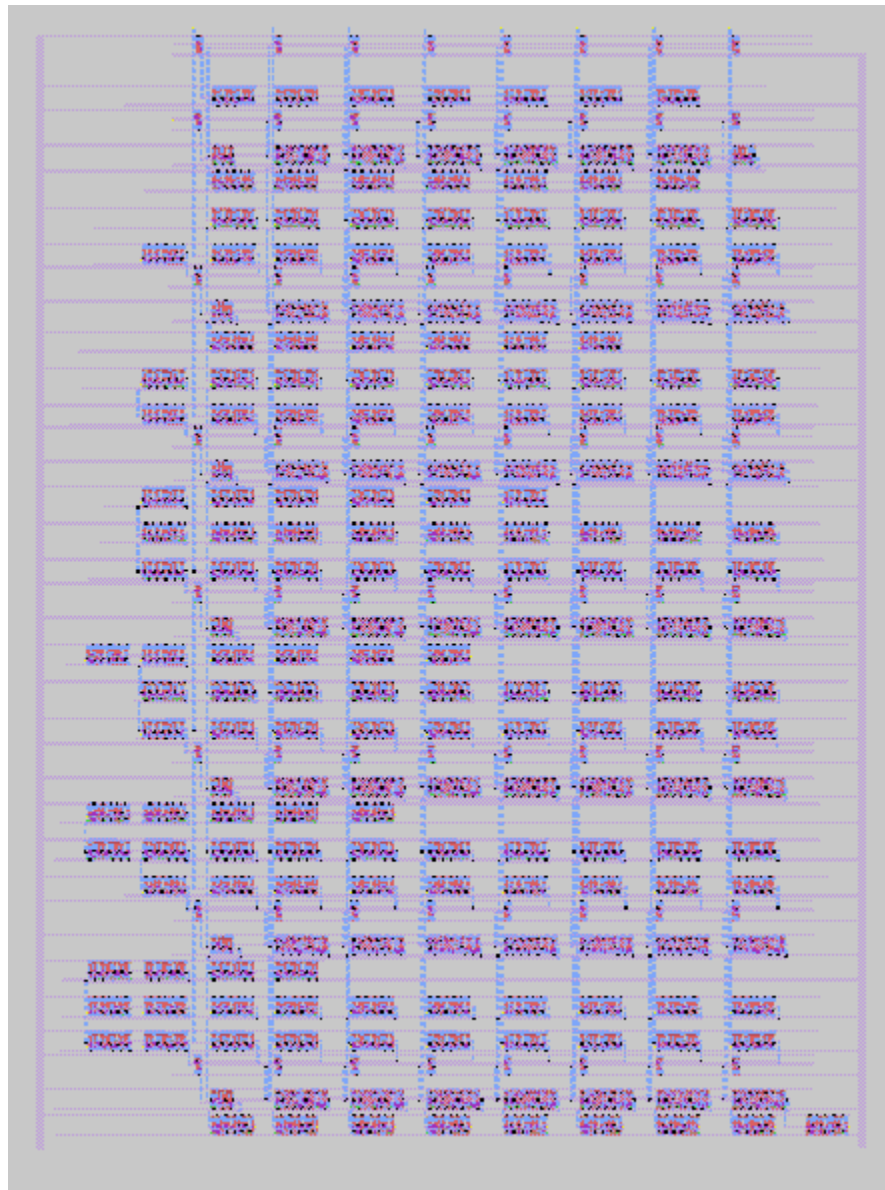Part II – Pipelined Layout Without Clock Routing




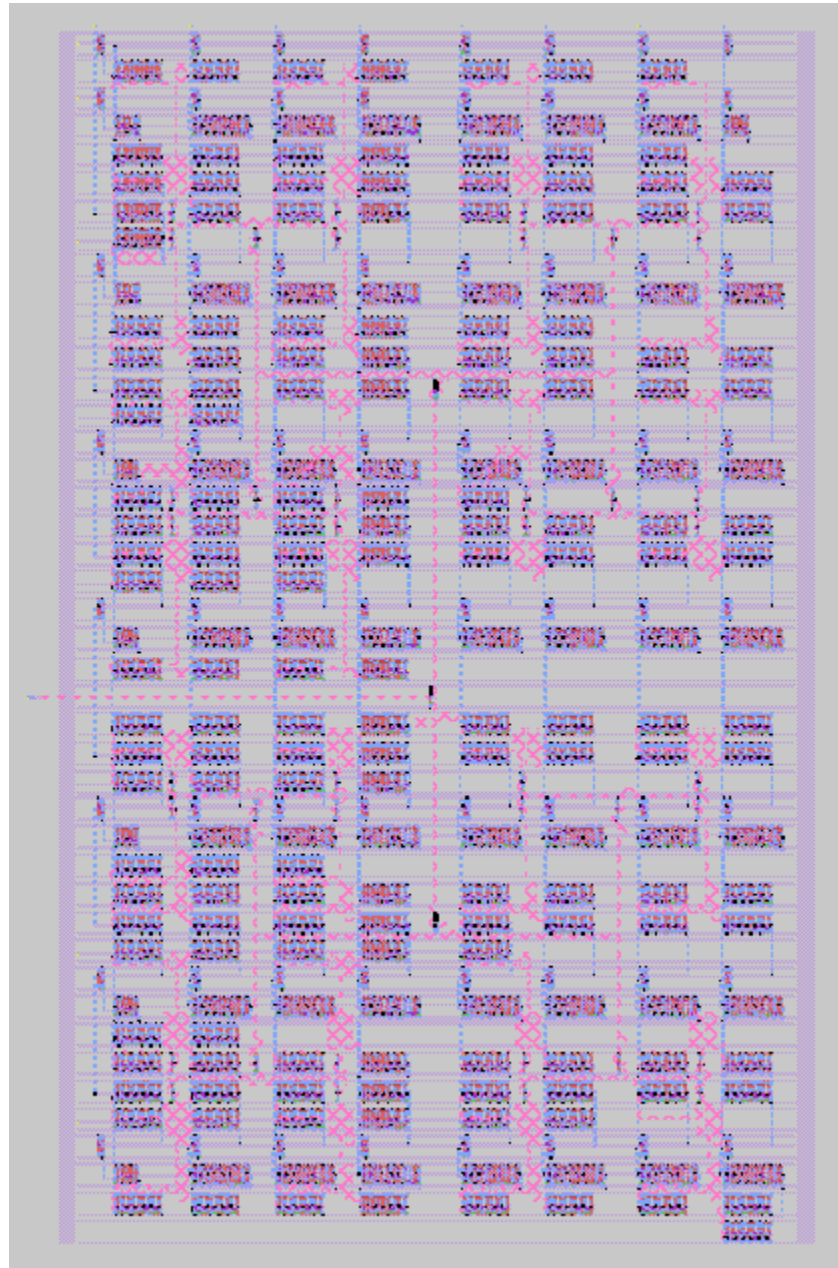
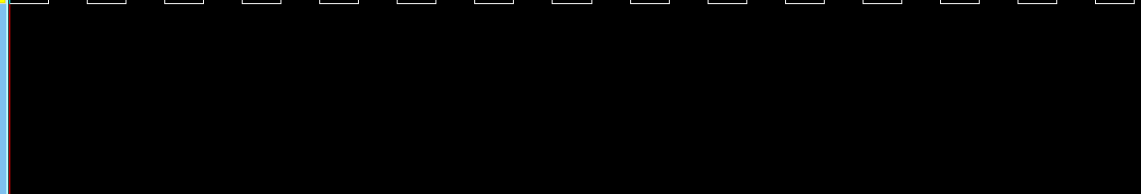
logic analyzer display

ZoomBaseWindowPrint

0.00														3000.00	
MULTPLICAND	0	1	2	3	4	5	6	7	8	9	10	11	12	13	
MULTIPLIER	1														
RESULT	???					0	1	2	3	4	5	6	7		
CLK!															

Part III – Pipelined Layout With Zero-Skew Clock Routing



0.00	2.56													3000.00	
MULTIPPLICAND	0	1	2	3	4	5	6	7	8	9	10	11	12	13	0
MULTIPLIER	1													1	
RESULT	???					0		1	2	3	4	5	6	???	
CLK														0	
															0
															0
															0
															0